

Components List

Component	Quantity	Note
Arduino UNO	1	Main controller
DFPlayer Mini	1	Voice playback
16x2 LCD (I2C module)	1	Display for messages
metal foil or copper dots	8	Trigger inputs
Resistors (10kΩ)	8	External pull-up resistors
Speaker (3W 8Ω)	1	Sound output
Power Supply	5V	Common power for all
Wires & Breadboard	—	For connections

Arduino ↔ I2C LCD (16x2)

LCD Pin	Arduino Pin	Description
VCC	5V	Power
GND	GND	Common ground
SDA	A4	I2C Data line
SCL	A5	I2C Clock line

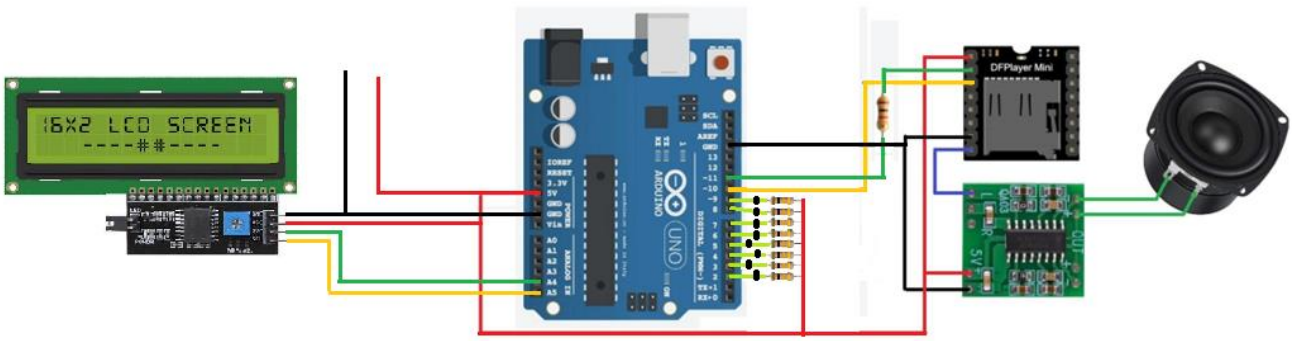


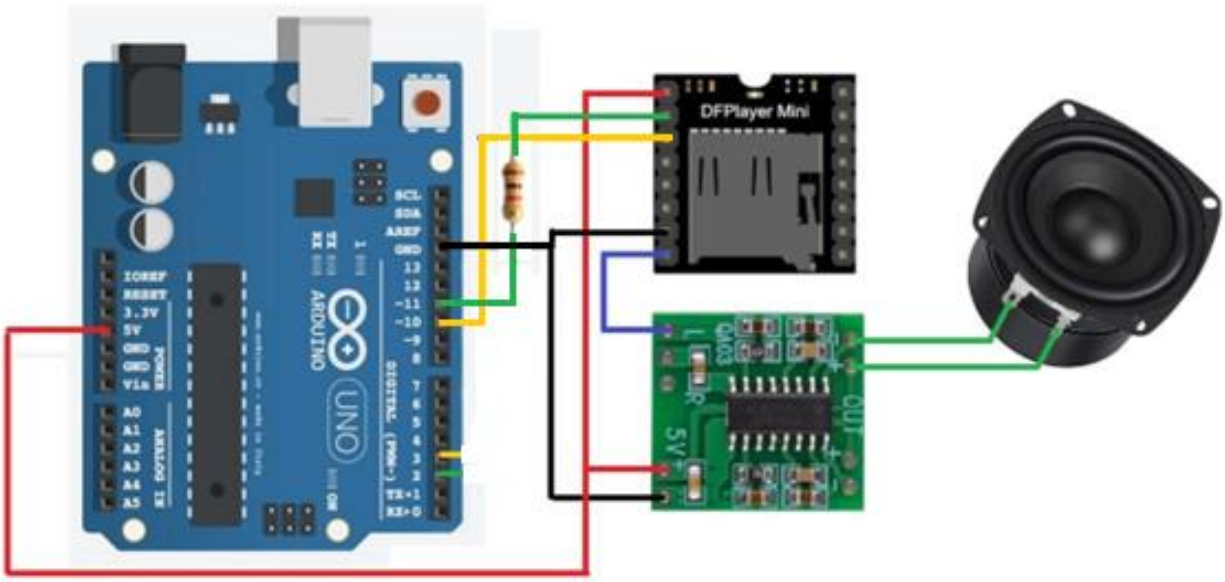

Touch Points with External Pull-Up

हर touch pad को Arduino के अलग-अलग pins से जोड़ें:

Touch Pad	Arduino Pin	Connection
Touc1h 1	D2	D2 → 10kΩ → +5V, pad → finger → GND
Touch 2	D3	D3 → 10kΩ → +5V, pad → finger → GND
Touch 3	D4	D4 → 10kΩ → +5V, pad → finger → GND
Touch 4	D5	D5 → 10kΩ → +5V, pad → finger → GND
Touch 5	D6	D6 → 10kΩ → +5V, pad → finger → GND
Touch 6	D7	D7 → 10kΩ → +5V, pad → finger → GND
Touch 7	D8	D8 → 10kΩ → +5V, pad → finger → GND
Touch 8	D9	D9 → 10kΩ → +5V, pad → finger → GND

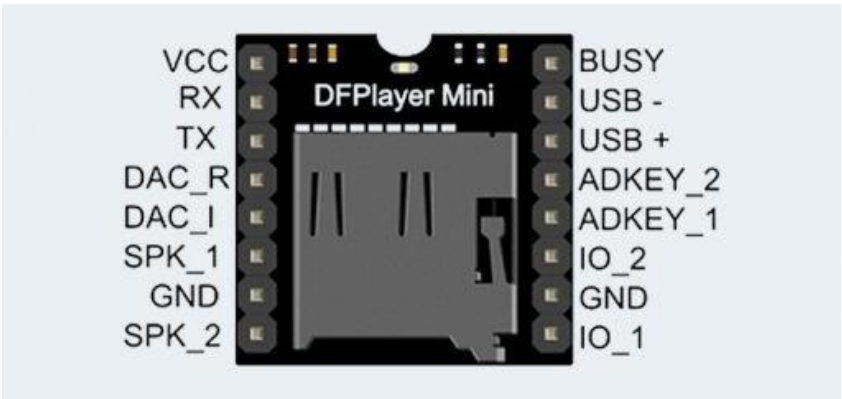

Arduino ↔ DFPlayer Mini Connection

DFPlayer Pin	Arduino Pin	Description
VCC	5V	Power input
GND	GND	Common ground
TX	D10	Data from DFPlayer to Arduino
RX	D11	Data from Arduino to DFPlayer
SPK2	Speaker	Amplifier

Note: Arduino GND और DFPlayer GND को *जरूर common* रखें।